

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER- III(NEW) EXAMINATION – WINTER 2022****Subject Code:3131102****Date:24-02-2023****Subject Name:Digital System Design****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	Marks
Q.1 (a) State and prove De-Morgan's Theorem.	03
(b) Differentiate between combinational and sequential circuits.	04
(c) Simplify the following Boolean expression by means of the Tabulation method. $F(A,B,C,D) = \sum m(1,2,5,6,7,8,9,11,12,13,15)$	07
Q.2 (a) Convert as below	03
I. $(110101010)_2 = ()_8 = ()_{16}$	
II. $(673.10)_8 = ()_2$	
III. $(ABF)_{16} = ()_{10}$	
(b) Show that NAND & NOR are universal gates	04
(c) Minimize the following function in SOP minimal form using K-Maps: $F(A, B, C, D) = \sum m(1, 2, 6, 7, 8, 13, 14, 15) + d(3, 5, 12)$	07
OR	
(c) Design a 4 bit binary to gray code converter and implement using EX-OR gates only.	07
Q.3 (a) Give comparison of TTL and CMOS family.	03
(b) Explain half adder & half subtractor circuit.	04
(c) Explain about JK & RS Flip Flop circuit using its symbol, block diagram, truth table and characteristics equation.	07
OR	
Q.3 (a) Derive excitation tables for R-S, J-K and T flip-flops.	03
(b) Compare ROM, PLA and PAL.	04
(c) Design a counter to generate the repetitive sequence 0,1,2,4,3,6.	07
Q.4 (a) Discuss general state machine architecture	03
(b) Implement the 8×1 MUX using two 4×1 MUX.	04
(c) Describe working principle of Programmable Logic Array with block diagrams.	07
OR	
Q.4 (a) Define: Register, Ripple counter, Synchronous counter.	03
(b) Implement Full Adder using 3×8 decoder.	04
(c) Explain the types Finite machines.	07

- Q.5** (a) Compare asynchronous and synchronous state machines. 03
(b) Implement T flip flop using D flip flop. 04
(c) Describe the operation of 4-bit bidirectional shift register with logic diagram. 07

OR

- Q.5** (a) Define: i) Fan-in ii) Fan-out iii) Propagation delay 03
(b) Explain working of Toggle flip-flop with characteristic table and logic diagram. 04
(c) Explain dual slope type A/D converter in detail. 07

GTUQuestionPapers.com