

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER- III(NEW) EXAMINATION – WINTER 2022****Subject Code:3131103****Date:27-02-2023****Subject Name:Network Theory****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	<b>MARKS</b>
<b>Q.1 (a)</b> Differentiate between an open circuit and a short circuit. Draw their characteristics in v-i plane.	<b>03</b>
<b>(b)</b> Discuss the following: (1) Linear and Non-Linear elements (2) Bilateral and Unilateral elements (3) Active and Passive elements (4) Lumped and Distributed Networks.	<b>04</b>
<b>(c)</b> The figure:1 shows three windings on a magnetic core. Using different shaped dots, establish polarity markings for the windings, and write KVL equations for this network.	<b>07</b>
<b>Q.2 (a)</b> How many types of controlled sources are possible? Draw their symbols.	<b>03</b>
<b>(b)</b> How are ideal current and voltage sources defined? Show the conversion of a voltage source into a current source and vice versa.	<b>04</b>
<b>(c)</b> Find the current $I_1$ and $I_2$ in the network of figure:2 using mesh analysis.	<b>07</b>
<b>OR</b>	
<b>(c)</b> In the network of figure:3, use node analysis to determine $i_x$ .	<b>07</b>
<b>Q.3 (a)</b> How the following elements will behave at $t=0$ and $t=\infty$ . (1) Resistance (2) Inductor (3) Capacitor.	<b>03</b>
<b>(b)</b> An exponential voltage $v(t) = 4 e^{-5t}$ is applied at time $t=0$ to a series R-C circuit having $R= 0.2\Omega$ and $C=1F$ . Obtain current $i(t)$ through the circuit.	<b>04</b>
<b>(c)</b> Explain how to obtain the transient response of a first order system using an appropriate example.	<b>07</b>
<b>OR</b>	
<b>Q.3 (a)</b> What is time constant? What is its significance?	<b>03</b>
<b>(b)</b> Define the terms critical resistance, damping ratio, natural frequency and settling time for a series R-L-C circuit.	<b>04</b>
<b>(c)</b> In the network of figure:4, a steady state is reached with the switch k open. At $t=0$ , the switch is closed. Find the voltage across capacitor for $t>0$ .	<b>07</b>
<b>Q.4 (a)</b> Obtain Laplace transform of (1) Unit Step function (2) Unit Ramp function (3) Unit Impulse function.	<b>03</b>
<b>(b)</b> State (1) Millman's theorem (2) Maximum Power Theorem.	<b>04</b>
<b>(c)</b> State and explain maximum power transfer theorem. Also derive the condition for maximum power transfer to the load for DC and AC circuit.	<b>07</b>
<b>OR</b>	
<b>Q.4 (a)</b> Obtain Laplace transform of (1) $u(t - a)$ (2) $r(t - a)$ (3) $\delta(t - a)$ .	<b>03</b>

(b) State (1) Reciprocity Theorem (2) Superposition's theorem. 04

(c) Find the Norton's equivalent circuit at the terminals A-B of the circuit shown in figure:5. 07

Q.5 (a) Define (1) Graph (2) Cut-set (3) incidence matrix. 03

(b) Test whether the following polynomial is Hurwitz or not :  $s^3 + 4s^2 + 5s + 2$ . 04

(c) (1) Determine y-parameters in terms of h-parameters. 07  
 (2) Determine z-parameters in terms of h-parameters.

OR

Q.5 (a) Define (1) Oriented graph (2) Tieset matrix (3) Node. 03

(b) Determine the range of values of 'K' so that the polynomial  $P(s) = s^3 + 3s^2 + 2s + K$  is Hurwitz. 04

(c) (1) Determine h-parameters in terms of z-parameters. 07  
 (2) Determine h-parameters in terms of y-parameters.

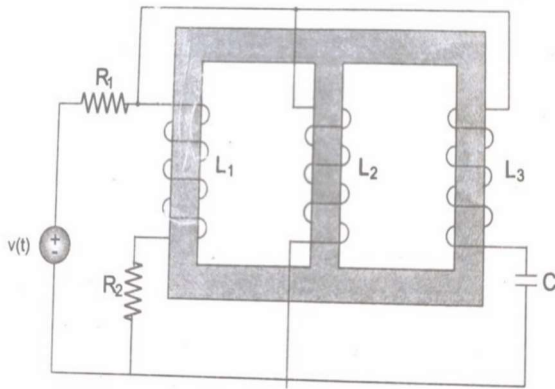


Figure:1

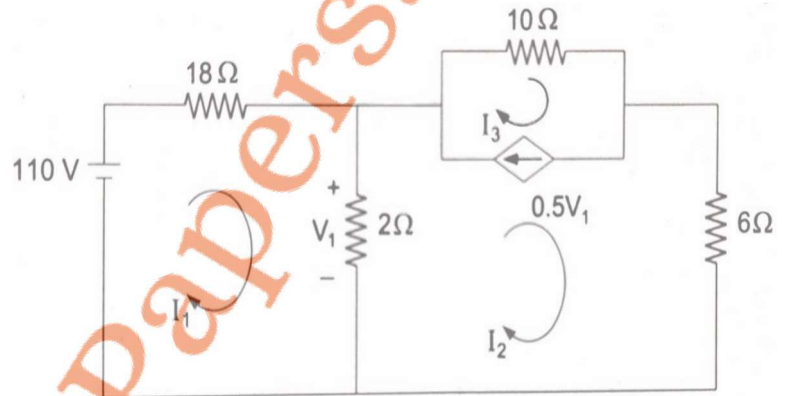


Figure:2

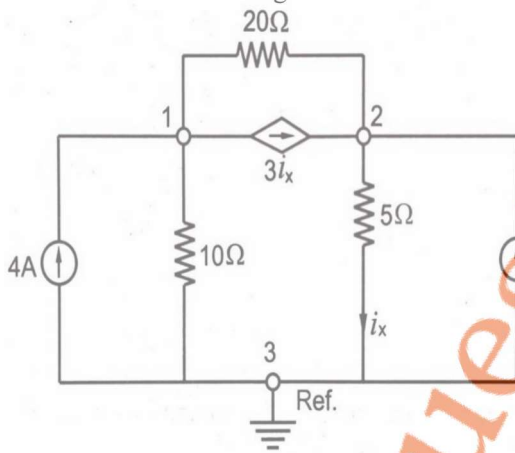


Figure:3

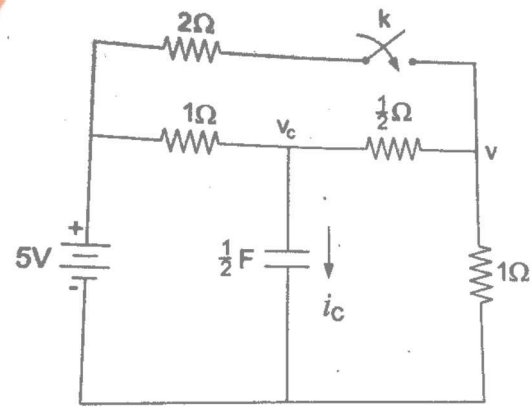


Figure:4

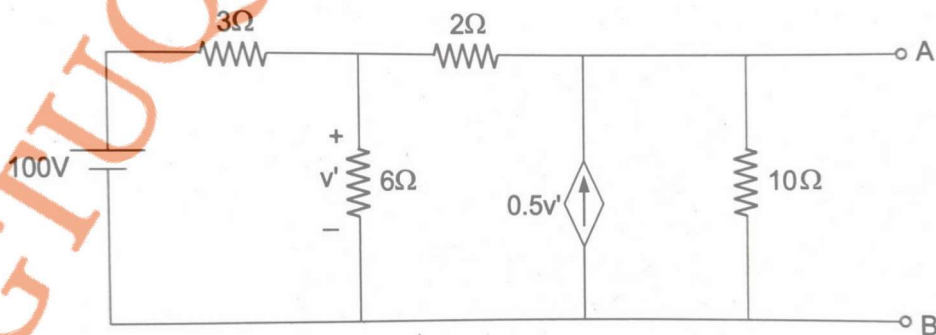


Figure:5