


**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-III(NEW) EXAMINATION – SUMMER 2023****Subject Code:3131103****Date:01-08-2023****Subject Name:Network Theory****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

|           |  | MARKS |
|-----------|--|-------|
| Q.1       | (a) Explain Ideal and Practical Current and Voltage sources with their characteristics and differentiate them with respect to ideality and practice. | 03    |
|           | (b) Briefly describe active, passive, lumped and distributed elements.   | 04    |
|           | (c) In the network of Fig-1, the switch k is closed at t=0 and the circuit was in steady state before. Determine particular solution of current i.   | 07    |
| Q.2       | (a) State the possible types of controlled sources and draw their symbols.   | 03    |
|           | (b) Define: Tree, Connected Graph, Co-tree, Sub-graph.   | 04    |
|           | (c) Determine current through 4 Ω resistor using mesh analysis for network of Fig-2.   | 07    |
| <b>OR</b> |  |       |
|           | (c) State and explain maximum power transfer theorem with necessary derivation.  | 07    |
| Q.3       | (a) Explain Initial and final conditions of R, L and C elements.   | 03    |
|           | (b) Discuss rules for source transformation.   | 04    |
|           | (c) For the network of Fig-3, obtain current through 1 Ω resistor using Thevenin's theorem.  | 07    |
| <b>OR</b> |  |       |
| Q.3       | (a) Define time constant and state its importance in circuit analysis.   | 03    |
|           | (b) State and explain Norton's theorem with an example.  | 04    |
|           | (c) Determine voltage across 6Ω resistor of Fig-4 using node analysis.   | 07    |
| Q.4       | (a) Explain dot convention for coupled coils with suitable example.  | 03    |
|           | (b) Give statements for Reciprocity Theorem and Superposition Theorem.   | 04    |
|           | (c) Find values of $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at t=0+ . for the network of Fig-5, if switch k is changed from position 1 to 2 at t=0.     | 07    |
| <b>OR</b> |  |       |
| Q.4       | (a) Derive ABCD parameters in terms of z-parameters.   | 03    |
|           | (b) Determine h-parameters in terms of y-parameters.   | 04    |
|           | (c) Derive relationship between incidence matrix, fundamental tie-set matrix and fundamental cut-set matrix.   | 07    |
| Q.5       | (a) Define: oriented graph, node, tie-set matrix.  | 03    |
|           | (b) Determine h-parameters in terms of z-parameters.   | 04    |
|           | (c) Determine h parameters for network of Fig-6  | 07    |

**OR**

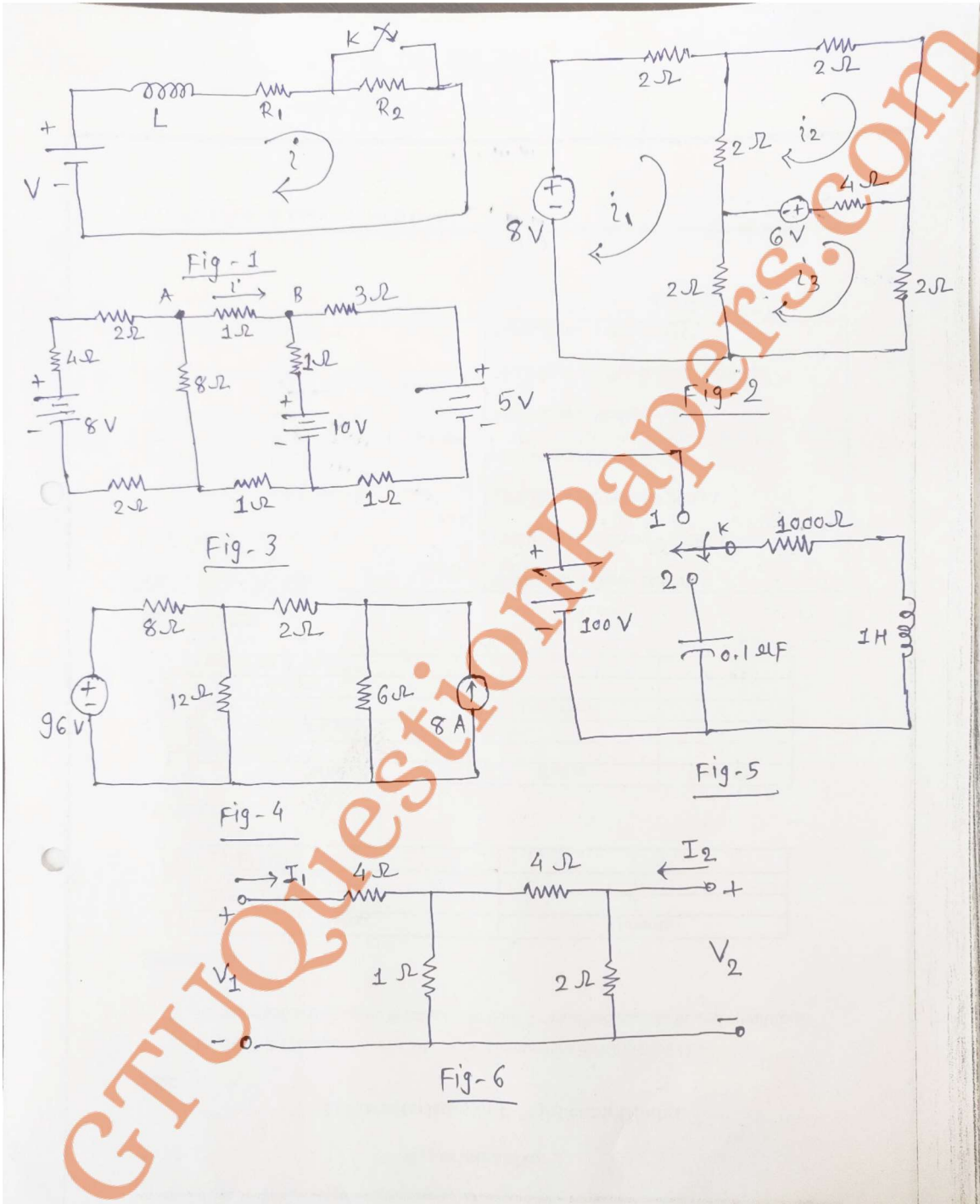- Q.5 (a) Define: Incident Matrix, cut-set, graph. 03  
 (b) Briefly explain PRF. 04  
 (c) Derive the condition for the network to be symmetrical for g-parameters. 07



\*\*\*\*\*