

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-IV (NEW) EXAMINATION – WINTER 2021****Subject Code:3141002****Date:31/12/2021****Subject Name:Analog Circuit Design****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	MARKS
Q.1 (a) Define following terms. SVRR, Slew Rate, CMRR.	03
(b) List ideal characteristics of OP-AMP.	04
(c) Explain inverting integrator circuit using OP-AMP.	07
Q.2 (a) Derive gain expression for voltage shunt F/B amplifier using OP-AMP.	03
(b) Explain peak detector using OP-AMP.	04
(c) Write and explain differential amplifier using three OP-AMP.	07
OR	
(c) Explain Instrumentation amplifier circuit operation using OP-AMP.	07
Q.3 (a) Explain circuit made up of OP-AMP that does addition of inputs.	03
(b) Explain 1 st order low pass filter using OP-AMP.	04
(c) Explain 2 nd order high pass filter using OP-AMP with derivations.	07
OR	
Q.3 (a) Define following terms. Lock Range for PLL, Capture Range for PLL, Frequency Stability for Oscillators.	03
(b) Explain class A power amplifier.	04
(c) Draw and explain square wave generator using OP-AMP.	07
Q.4 (a) Explain grounded load V to I converter using OP-AMP.	03
(b) Explain Wien bridge oscillator using OP-AMP in detail.	04
(c) Explain CE short-circuit current gain without resistive load R_L .	07
OR	
Q.4 (a) Explain voltage limiter circuit using OP-AMP with suitable example.	03
(b) Draw and explain class B push pull power amplifier.	04
(c) Derive expression for trans-conductance g_m in Hybrid – Π model.	07
Q.5 (a) Design Monostable multivibrator for $T_P = 1.1$ millisecond, take $C = 0.1$ milliferad.	03
(b) Write short note on voltage regulator.	04
(c) Explain 555 Monostable multivibrator.	07
OR	
Q.5 (a) Explain sample and hold circuit using OP-AMP.	03
(b) Design A-stable multivibrator using IC 555 for $T_{on} = 50\%$ of T , take $F = 1$ KHz, $C = 0.1$ milliferad.	04
(c) Explain A-stable multivibrator using IC 555.	07
