

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-IV(NEW) EXAMINATION – WINTER 2022****Subject Code:3141002****Date:13-12-2022****Subject Name:Analog Circuit Design****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	MARKS
Q.1 (a) Define following terms. CMRR, PSRR, Slew Rate.	03
(b) Explain Voltage Transfer Curve of OP-AMP.	04
(c) Write and explain differential amplifier using two OP-AMP.	07
Q.2 (a) List OP-AMP's ideal characteristics.	03
(b) Derive gain expression for voltage series F/B amplifier using OP-AMP.	04
(c) Explain inverting differentiator circuit using OP-AMP.	07
OR	
(c) Explain instrumentation amplifier circuit operation using OP-AMP.	07
Q.3 (a) Explain circuit made up of OP-AMP that does average of inputs.	03
(b) Explain Schmitt trigger circuit using OP-AMP.	04
(c) Explain 2 nd order low pass filter using OP-AMP with derivations.	07
OR	
Q.3 (a) Define following terms. Lock Range for PLL, Capture Range for PLL, Frequency Stability for Oscillators.	03
(b) Explain class B power amplifier.	04
(c) Draw and explain triangular wave generator using OP-AMP.	07
Q.4 (a) Explain floating load V to I converter using OP-AMP.	03
(b) Explain phase shift oscillator using OP-AMP in detail.	04
(c) Explain CE short-circuit current gain with resistive load R_L .	07
OR	
Q.4 (a) Explain sample hold circuit using OP-AMP.	03
(b) Draw and explain class AB power amplifier.	04
(c) Derive expression for trans-conductance g_m in Hybrid – Π model.	07
Q.5 (a) Design Monstable multivibrator using timer IC for $T_P = 11$ millisecond, take $C = 0.1$ microferad.	03
(b) Write short note on voltage regulator.	04
(c) Explain A-stable multivibrator using timer IC.	07
OR	
Q.5 (a) Explain half wave rectifier circuit using OP-AMP.	03
(b) Design A-stable multivibrator using IC 555 for $T_{on} = 75\%$ of T , take $F = 1$ KHZ, $C = 0.1$ microferad.	04
(c) Explain monostable multivibrator using IC 555.	07
