

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-IV (NEW) EXAMINATION – WINTER 2023****Subject Code:3141002****Date:11-01-2024****Subject Name:Analog Circuit Design****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	MARKS
<b>Q.1</b> (a) List all the characteristics of an ideal OP-AMP.	<b>03</b>
(b) Explain how and why does trans-conductance varies with increasing $ I_c $ , $ V_{CE} $ and Temperature at high frequency.	<b>04</b>
(c) You are given a set of components as follows: Resistors- 2.2 k $\Omega$ (2), 3.9k $\Omega$ (2), 4.7k $\Omega$ (2) a capacitor-0.1 $\mu$ F and an IC555.Design an astable multi-vibrator with free running frequency of approximately 1 kHz. Draw the final design with pin connections and values of each component chosen by you as your answer. Also, show all the calculations related to your design.	<b>07</b>
<b>Q.2</b> (a) Give full forms of: CMRR, PSRR, PLL	<b>03</b>
(b) Explain the concept of virtual ground and discuss how it is different from actual ground.	<b>04</b>
(c) Derive an expression for the short circuit current gain for the hybrid- $\pi$ model in CE configuration.	<b>07</b>
<b>OR</b>	
(c) Derive an expression for emitter diffusion capacitance in terms of base width, diffusion constant and trans-conductance for the hybrid- $\pi$ model in CE configuration.	<b>07</b>
<b>Q.3</b> (a) Give full forms: ADC, HPF, VCO	<b>03</b>
(b) Compare Class A and Class B amplifiers.	<b>04</b>
(c) Derive an expression for the frequency of oscillations for the Wein bridge oscillator.	<b>07</b>
<b>OR</b>	
<b>Q.3</b> (a) What is an electronic filter? List all types of electronic filters.	<b>03</b>
(b) Compare current series feedback with current shunt feedback.	<b>04</b>
(c) A CE amplifier with an un-bypassed emitter resistance providing current series feedback to be designed for trans-conductance gain of -1 mA/V, voltage gain of -4 and a desensitivity of 50. If $R_s=1K\Omega$ , $h_{fe}=150$ and $r_{bb}$ is negligible, find (i) $R_e$ , (ii) $R_L$ ,(iii) $R_{if}$ and (d) $I_{C(quietent)}$ .	<b>07</b>
<b>Q.4</b> (a) Define: Slew rate, Input bias current, Input offset current	<b>03</b>
(b) Explain the working of Class AB amplifier in brief.	<b>04</b>
(c) A Second Order Low Pass Filter is to be designed around a non-inverting op-amp with equal resistor and capacitor values in its cut-off frequency determining circuit. If the filters characteristics are given as: quality factor $Q = 5$ , andcorner frequency $f_c = 159\text{Hz}$ , design a suitable low pass filter. Assume $R=10\text{ k}\Omega$ .	<b>07</b>

**OR**

- Q.4** (a) In the Colpitts oscillator,  $C_1=0.2 \mu\text{F}$   $C_2=0.02 \mu\text{F}$ . If the frequency of oscillation required is 10 kHz, find the value of inductor. **03**  
(b) Explain Barkhausen criterion for oscillations. **04**  
(c) Describe the complete process of state variable filter design in details. **07**

- Q.5** (a) Give full forms: ECL, VCVS, GBP **03**  
(b) Give complete classification of oscillators. **04**  
(c) Derive the expressions for the voltage gain and input resistance with feedback for an emitter follower circuit. **07**

**OR**

- Q.5** (a) Calculate the frequency of oscillations for an RC phase shift oscillator given  $R=10\text{K}\Omega$  and  $C=0.1 \mu\text{F}$ . **03**  
(b) For a non-inverting OP-AMP summing circuit with inputs of 1V, 2V and 3V, respectively,  $R_f=2\text{K}\Omega$  and  $R_{in}=1\text{K}\Omega$ . Determine output voltage. **04**  
(c) Design an adjustable voltage regulator using LM317 to satisfy the following specifications: **07**  
Output Voltage=5 to 12 V, Output current=1.0 A.  $I_{ADJ}=100 \mu\text{A}$ .  
Assume  $R_1=240\Omega$ .

\*\*\*\*\*

GTU Question Papers.com