

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER- III(NEW) EXAMINATION – WINTER 2022****Subject Code:3130704****Date:27-02-2023****Subject Name:Digital Fundamentals****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- |   | <b>Marks</b> |
|---|--------------|
| <b>Q.1 (a)</b> Implement NOR, AND, & OR gates using NAND gates only   | <b>03</b>    |
| <b>(b)</b> Write the boolean expression for the logic diagram given below and simplify it as much as possible and draw the logic diagram that implements the simplified expression  | <b>04</b>    |
|   |              |
| <b>(c)</b> Do as directed:  | <b>07</b>    |
| 1. Convert $(75.75)_{10} = (\quad)_8 = (\quad)_{16}$  |              |
| 2. Convert $(101.10)_{16} = (\quad)_8$  |              |
| 3. Add $(17)_{10}$ and $(-25)_{10}$ using 8-bit 2's complement  |              |
| <b>Q.2 (a)</b> Explain SR flip-flop using characteristic table & characteristic equation  | <b>03</b>    |
| <b>(b)</b> Explain 4-bit parallel binary adder with neat and clean diagram  | <b>04</b>    |
| <b>(c)</b> Obtain the set of prime implicants for Function $F = \sum m(1,2,3,5,6,7,8,9,12,13,15)$   | <b>07</b>    |
| <b>OR</b>   |              |
| <b>(c)</b> A combinational logic circuit is defined by the functions:<br>$F_1 = \sum (0,1,2,4)$ and $F_2 = \sum (0, 5, 6,7)$ .<br>Implement the circuit with a PLA having three inputs, four product terms and two outputs. | <b>07</b>    |
| <b>Q.3 (a)</b> Differentiate synchronous counter and asynchronous counter   | <b>03</b>    |
| <b>(b)</b> Explain BCD adder using two 4-bit adder IC and a correction -detector circuit  | <b>04</b>    |
| <b>(c)</b> Do the conversion of JK flip flop to T flip flop and D flip flop to JK   | <b>07</b>    |
| <b>OR</b>   |              |
| <b>Q.3 (a)</b> Design 4 X 16 decoder using two 3 X 8 decoders   | <b>03</b>    |
| <b>(b)</b> List and explain in detail Binary codes with example   | <b>04</b>    |
| <b>(c)</b> Design mod-6 asynchronous counter using T flip flop  | <b>07</b>    |
| <b>Q.4 (a)</b> Reduce the expression $\sum (2, 3, 6,7,8,10,11,14)$ using K-map  | <b>03</b>    |

- (b) Do as directed: 04  
1. Add 25+17 in BCD  
2. Add 37 +28 in XS-3

- (c) With a neat block diagram explain the function of encoder. Explain priority encoder? 07

**OR**

- Q.4** (a) Explain R-2R ladder type D/A converter 03

- (b) Implement the following Boolean functions with a 3 x 1 multiplexer F (w, x, y, z) =  $\Sigma$  (2, 3, 5, 6, 11, 14, 15) 04

- (c) Design Combinational circuit for Binary to XS-3 conversion 07

- Q.5** (a) Compare TTL, ECL, & CMOS logic families. 03

- (b) Draw truth table of 2-bit digital comparator 04

- (c) List out various commonly used D/A converters. Draw & explain any one D/A converter. 07

**OR**

- Q.5** (a) A combinational logic circuit is defined by the functions: 03  
 $F_1 = \Sigma$  (0,1,2,5,7) and  $F_2 = \Sigma$  (1, 2,4, 6). Implement the circuit with a PROM

- (b) Explain types of shift-register and their application 04

- (c) List out various commonly used A/D converters. Draw & explain any one A/D converter 07