

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER- IV EXAMINATION – SUMMER 2020****Subject Code: 3141706****Date: 26/10/2020****Subject Name: Analog Signal Processing****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
<b>Q.1</b>	(a) Define Following terms:	<b>03</b>
	1. CMRR	
	2. SVRR	
	3. Slew Rate	
	(b) Draw and explain in brief the internal block diagram of an Op-Amp.	<b>04</b>
	(c) Derive the equation of voltage gain of differential amplifier using one Op-Amp (Closed loop configuration) with its circuit diagram.	<b>07</b>
<b>Q.2</b>	(a) Draw and explain Voltage follower circuit using an Op-Amp.	<b>03</b>
	(b) Explain Bandwidth and Total output offset voltage for Inverting Amplifier with feedback.	<b>04</b>
	(c) Derive the equation of voltage gain of Non-Inverting Summing amplifier using an Op-Amp with its circuit diagram.	<b>07</b>
<b>OR</b>		
	(c) Draw and explain Voltage to Current converter with floating load using an Op-Amp.	<b>07</b>
<b>Q.3</b>	(a) Explain Subtractor circuit using an Op-amp.	<b>03</b>
	(b) Explain Zero Crossing detector circuit using an Op-Amp with input/output waveforms.	<b>04</b>
	(c) Explain Practical Differentiator circuit using an Op-Amp with its circuit diagram. Frequency response, input/output waveforms.	<b>07</b>
<b>OR</b>		
<b>Q.3</b>	(a) Draw and Explain Voltage limiter circuit using an Op-Amp.	<b>03</b>
	(b) Draw and explain Sample and Hold circuit using an Op-Amp.	<b>04</b>
	(c) Draw Op-amp based full wave rectifier (absolute value output) circuit. Explain its working with necessary input/output waveforms.	<b>07</b>
<b>Q.4</b>	(a) Design + 5V power supply using 7805 with its circuit diagram	<b>03</b>
	(b) Explain adjustable voltage regulator using LM 317.	<b>04</b>

- (c) Explain Instrumentation Amplifier using three Op-Amp Configuration and also derive the equation for the output voltage. **07**

**OR**

- Q.4** (a) Explain Voltage controlled Oscillator (VCO) using IC 566. **03**  
(b) Draw and explain Square wave generator circuit using an Op-Amp. **04**  
(c) Explain Successive Approximation type Analog to Digital **07**

- Q.5** (a) Explain All Pass filter. **03**  
(b) Draw and explain Programmable Gain Amplifier. **04**  
(c) Explain first order Low pass Butterworth Active filter with circuit diagram and derivation of its transfer function. **07**

**OR**

- Q.5** (a) Explain Notch filter with its circuit diagram and necessary waveforms. **03**  
(b) Explain Ramp Generator circuit using 555 timer in Astable mode operation. **04**  
(c) Explain Monostable operation of 555 timer with its internal block diagram with its output voltage and capacitor voltage waveforms. **07**

\*\*\*\*\*