

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE- SEMESTER-IV (NEW) EXAMINATION – WINTER 2020**

**Subject Code:3141706****Date:09/02/2021****Subject Name:Analog Signal Processing****Time:02:30 PM TO 04:30 PM****Total Marks:56****Instructions:**

1. Attempt any FOUR questions out of EIGHT questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain the following terms: **02**  
       1) CMRR **01**  
       2) Input Bias Current **04**  
 (b) Define Input Offset Voltage and Slew Rate **07**  
 (c) Describe the basic integrator circuit using opamp. Mention the problems associated with the basic integrator and the methods to eliminate them. Also derive the formula for  $f_b$  and  $f_a$ . **07**
- Q.2** (a) Explain the working of the I-V converter circuits with necessary derivations **03**  
 (b) Explain the working of the V-I converter circuit with grounded load with necessary derivations. **04**  
 (c) Define Negative Feedback. Mention all the four basic configurations for negative feedback. Describe opamp in voltage series configuration and derive the expression for closed loop voltage gain. **07**
- Q.3** (a) Explain the working of Sample and Hold circuit with necessary diagrams. **03**  
 (b) Explain positive and negative clippers with necessary diagrams. **04**  
 (c) Explain the working of D/A converter with Binary weighted resistors. **07**
- Q.4** (a) Explain positive clippers with necessary diagrams. **03**  
 (b) Explain the working of Schmitt Trigger circuits with necessary diagrams and derivations. **04**  
 (c) Explain the working of D/A converter with R-2R ladder network. **07**
- Q.5** (a) Define instrumentation amplifier. where it is used? **03**  
 (b) Describe instrumentation amplifier using Resistive Transducer Bridge **04**  
 (c) Explain the working of 555 timer in Monostable mode with necessary equations and waveforms. **07**
- Q.6** (a) Explain Isolation amplifier. **03**  
 (b) Explain Logarithmic amplifier. **04**  
 (c) Explain the working of 555 timer as Astable multivibrator with necessary equations and waveforms. **07**
- Q.7** (a) Give the necessary conditions for sustaining oscillations. **03**  
 (b) Draw the circuit for Wein-Bridge oscillator and derive expression for output frequency of oscillation. **04**  
 (c) Describe 1<sup>st</sup> order active Butterworth low-pass filter and derive its transfer function. **07**

- Q.8** (a) Explain the working of Notch Filter. **03**
- (b) Design a Narrow Band-Pass filter such that  $f_c=1\text{Khz}$ ,  $Q=3$ ,  $A_f=10$ . Assume the value of capacitors to be  $0.01\mu\text{F}$ . **04**
- (c) Explain Square wave generator using opamp. Using it, explain how we can generate a triangular wave. **07**

\*\*\*\*\*

GTUQuestionPapers.com