

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-III (NEW) EXAMINATION – WINTER 2020****Subject Code:3130704****Date:05/03/2021****Subject Name:Digital Fundamentals****Time:10:30 AM TO 12:30 PM****Total Marks:56****Instructions:**

1. Attempt any FOUR questions out of EIGHT questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

	MARKS
Q.1 (a) Realize AND, OR and NOT gate using NAND gates only.	03
(b) State and prove De-Morgan's theorems using truth-tables.	04
(c) Do as directed:	07
(a) $(1111.11)_2 = (?)_8 = (?)_{10}$	
(b) $23 - 48$ using 2's complement method	
(c) $(396)_{10} = (?)_{BCD} = (?)_{EX-3}$	
(d) $(11111)_2 = (?)_{Gray}$	
Q.2 (a) Define following: Figure of merit, Noise margin, and Power dissipation.	03
(b) Construct Hamming code for BCD 0110. Use even parity.	04
(c) Given a logic function: $Z = ABC + BC'D + A'BC$.	07
(i) Make a truth table.	
(ii) Simplify using K-map.	
(iii) Realize simplified function using NAND gates only.	
Q.3 (a) Draw the logic diagram of 1-digit BCD adder.	03
(b) Minimize following Boolean function using K-map:	04
$Y(A,B,C,D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$	
(c) Write a brief note on race around condition and its solution. Draw & explain the logic diagram of master-slave JK flip-flop.	07
Q.4 (a) Draw truth table of 2-bit digital comparator.	03
(b) Minimize following Boolean function using K-map:	04
$F(A,B,C,D) = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$	
(c) Design a 4-bit synchronous down counter using T flip-flops.	07
Q.5 (a) Design D FF using SR FF. Write truth table of D FF.	03
(b) Draw & explain in brief the logic diagram of 4-bit bidirectional shift register.	04
(c) List out various commonly used D/A converters. Draw & explain any one D/A converter.	07
Q.6 (a) List out and explain any one application of the register.	03
(b) Design a 4-bit ripple up counter using JK flip-flops.	04
(c) List out various commonly used A/D converters. Draw & explain any one A/D converter.	07
Q.7 (a) Draw internal organization of a 16 x 4 memory chip.	03
(b) Write a brief note on quantization and encoding.	04
(c) Write a detailed note on various types of memories.	07

- Q.8** (a) List out various characteristics of a D/A converter. Discuss any one. **03**
(b) Obtain 2048 x 8 memory using 256 x 8 memory chips. **04**
(c) Draw and explain in detail the block diagram of CPLD. **07**

GTUQuestionPapers.com